AA 84 1 LOCKING 6.57

## ROYAL AIR FORCE—AIRCRAFT APPRENTICES No. 1 RADIO SCHOOL, LOCKING

INTERMEDIATE EXAMINATION IN EDUCATIONAL SUBJECTS SEPTEMBER, 1956 (84TH) ENTRY

JUNE, 1957

## BASIC RADIO PRINCIPLES

Time allowed—Three hours

SIX questions to be attempted

All questions carry equal marks



- (a) Figure 1 is the valve heater circuit of a universal receiver which is to be operated from a d.c. supply of 230 vorts. Each of the five valves is designed to take a heater current of 0.15 amp; their working voltages are as shown. The resistor R is to adjust the circuit current to 0.15 amp. Calculate:-
  - (i) the resistance of R (to the nearest ohm),
  - (ii) the power dissipated in R, and
  - (iii) the power taken from the supply.
- (b) It is desired to add a dial light to the circuit of Figure 1. The bulb to be used, rated at 7.5 volt, 0.1 amp, is to be wired in parallel with a resistor r, which is connected between V<sub>2</sub> and V<sub>3</sub>. The parallel resistor r is chosen so that the correct current is passed by the dial light. Calculate :-
  - (i) the resistance of r,
  - (ii) the power dissipated in r, and
  - (iii) the new value of R (to nearest ohm).
- (2) (a) On the same set of axes draw hysteresis loops for soft iron and steel.
  - (b) Explain the following terms, and by reference to the loops required at (a) above, compare their values for soft iron and steel-
    - (i) Remanence (Retentivity).
    - (ii) Coercivity.
  - (c) Give reasons why—

1.

- (i) self-excited dynamos have pole-pieces of high remanence;
- (ii) steel is far better than soft iron for the construction of permanent magnets;
- (iii) all modern audio-frequency magnetic materials have hysteresis loops of small area.



- 3.)(a) Explain with the aid of a diagram the action of a thermo-couple meter.
  - (b) What are the relative advantages and disadvantages of the thermo-meter over the moving-coil type for current measurement?
  - (c) A moving coil milliammeter of resistance 75 ohms and full scale deflection 1mA is to be converted for use as a 0-100 voltmeter.
    - (i) Draw a suitable circuit, and indicate the polarity of the meter and of the input to be measured.
    - (ii) Calculate the resistance and wattage of the multiplier to be used.
    - (iii) What is the sensitivity of this voltmeter?
- 4. (a) By reference to the magnetic field of a solenoid, explain why any variations in current through the solenoid are opposed.
  - (b) A coil of inductance 5 henry and resistance 10 ohms is connected through a switch to a d.c. supply of 20 volts. Explain, with the aid of a graph, and with reference to the time constant of the circuit, the sequence of current variations when the switch is closed for 5 seconds and then opened. Calculate:—
    - (i) the greatest value of circuit current,
    - (ii) the time constant of the circuit, and
    - (iii) the value of current 0.5 sec after the circuit is made.

(a) What is meant by:—

(i) the peak value of an alternating voltage?

(ii) the Root Mean Square value of an alternating current?

(iii) the Power Factor of a circuit?

- (b) Explain why the true power in a purely inductive circuit is zero whereas the apparent power is not zero.
- (c) A resistor of 1,000 ohms is connected in series with a generator of negligible internal resistance. If the output of the generator has a peak value of 200 volts and frequency of 50 c/s, calculate to the nearest mA the instantaneous value of circuit current 2.5 milliseconds after the voltage has reached a peak value.

6) A coil of inductance 300 µH and of radio-frequency resistance 5 ohms is connected in parallel with a capacitor of  $0.0003 \mu F$ . Calculate for this circuit:—

- (a) the resonant frequency (to the nearest kilocycle),
- (b) the dynamic resistance,
- (c) the O-factor at the resonant frequency, and
- (d) the bandwidth.

- 00°.075 6:28